

# Introduction to Logic Design

## EEF205E

### Homework 5

Rüzgar Erik  
040240783

Istanbul Technical University  
Faculty of Electrical and Electronics Engineering

January 11, 2025

## Question 1

Recalling the JK flip-flop equations we can derive  $A(t+1)$  and  $B(t+1)$  as follows:

$$Q(t+1) = J \cdot \overline{Q} + \overline{K} \cdot Q \quad (1)$$

For the A flip-flop:  $J_A = x$  and  $K_A = b$

$$A(t+1) = x \cdot \overline{A} + \overline{b} \cdot A \quad (2)$$

For the B flip-flop:  $J_B = x$  and  $K_B = \overline{a}$

$$B(t+1) = x \cdot \overline{B} + a \cdot B \quad (3)$$

Given that there are 2 flip-flops there are  $2^2 = 4$  states and we can write the state transition table as follows:

Table 1: State Transition Table

Present State			Next State	
A	B	x	A(t+1)	B(t+1)
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	0	1
1	1	1	0	1

We can draw the state diagram as follows:

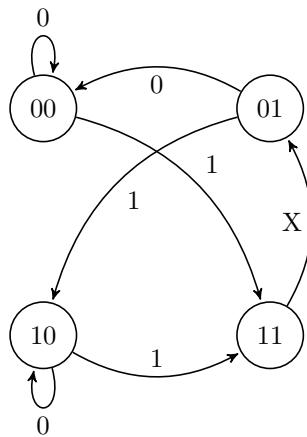


Figure 1: State Diagram

## Question 2

The logic diagram for the state machine can be drawn as follows:

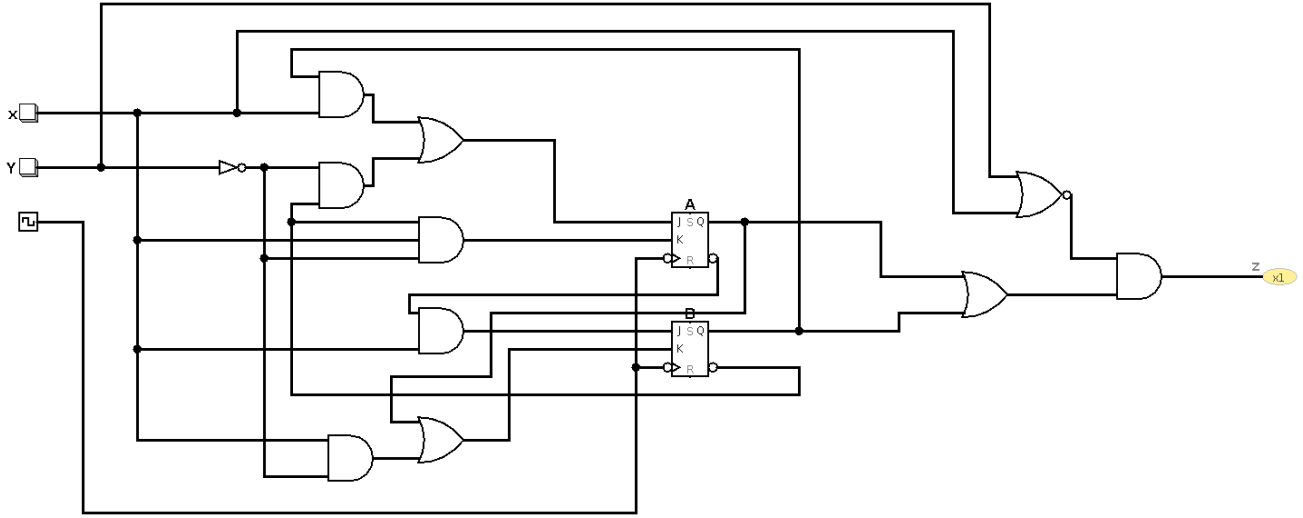


Figure 2: Logic Diagram for the State Machine

The state table can be written as follows:

Figure 3: State Table

Present State				Next State		
A	B	x	y	A*	B*	z
0	0	0	0	1	0	0
0	0	0	1	0	0	0
0	0	1	0	1	1	0
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	1	0
1	0	0	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	0
1	0	1	1	1	0	0
1	1	0	0	1	0	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	0	0

Recalling the JK flip-flop equations we can derive  $A(t+1)$  and  $B(t+1)$  as follows:

$$Q(t+1) = J \cdot \overline{Q} + \overline{K} \cdot Q \quad (4)$$

For the A flip-flop:

$$A^* = (b \cdot x + b' \cdot y') \cdot A' + (b + x' + y) \cdot A \quad (5)$$

$$B^* = (a' \cdot x) \cdot B' + [a' \cdot (x' + y)] \cdot B \quad (6)$$

# 1 Question 3

## Part A

The state table for the requested circuit can be written as follows:

Table 2: State Table

Present State			Next State	
A	B	x	A(t+1)	B(t+1)
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	1
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

To design the circuit with D Flip Flops We need its excitation table:

Table 3: D Flip-Flop Excitation Table

Present State	Next State	D Input
0	0	0
0	1	1
1	0	0
1	1	1

It can be seen that the equation for the D flip-flop is  $D = Q(t+1)$  so we can take the next state values from the state table and write the D values as follows:

Table 4: State Table

Present State			Next State		D Inputs	
A	B	x	A(t+1)	B(t+1)	D_A	D_B
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	1	0	1
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	0	0	0	0
1	1	0	1	1	1	1
1	1	1	1	0	1	0

We can find equations for  $D_A$  and  $D_B$  with the help of kmaps:

		$x$	
		0	1
$AB$	00	0	0
	01	0	1
	11	1	1
	10	1	0

Figure 4: K-Map for D\_A

The simplified equation for  $D_A$  is:

$$D_A = (\overline{x_{in}} \cdot A) + (x_{in} \cdot B) \quad (7)$$

We can draw the K-Map for  $D_B$  as follows:

		$x$	
		0	1
$AB$	00	0	1
	01	1	1
	11	1	0
	10	0	0

Figure 5: K-Map for D\_B

The simplified equation for  $D_B$  is:

$$D_B = (\overline{x_{in}} \cdot B) + (x_{in} \cdot \overline{A}) \quad (8)$$

All of the equations can be implemented in a circuit as follows:

$$D_A = (\overline{x_{in}} \cdot A) + (x_{in} \cdot B) \quad (9)$$

$$D_B = (\overline{x_{in}} \cdot B) + (x_{in} \cdot \overline{A}) \quad (10)$$

## Part B

The state table for the requested circuit can be written as follows:

Table 5: State Table

Present State			Next State	
A	B	x	A(t+1)	B(t+1)
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	0	1

Again using the principle of D flip-flops we can add the D inputs to the state table as follows:

Table 6: State Table

Present State			Next State		D Inputs	
A	B	x	A(t+1)	B(t+1)	D_A	D_B
0	0	0	0	0	0	0
0	0	1	1	1	1	1
0	1	0	0	1	0	1
0	1	1	1	0	1	0
1	0	0	1	0	1	0
1	0	1	0	0	0	0
1	1	0	1	1	1	1
1	1	1	0	1	0	1

We can find equations for  $D_A$  and  $D_B$  with the help of kmaps:

		$x$	
		0	1
$AB$	00	0	1
	01	0	1
	11	1	0
	10	1	0

Figure 6: K-Map for D\_A

The simplified equation for  $D_A$  is:

$$D_A = (\overline{x_{in}} \cdot A) + (x_{in} \cdot \overline{A}) \quad (11)$$

This shows an XOR gate is needed for the implementation of  $D_A$ .

$$D_A = x_{in} \oplus A \quad (12)$$

We can draw the K-Map for  $D_B$  as follows:

		$x$	
		0	1
$AB$	00	0	1
	01	1	0
	11	1	1
	10	0	0

Figure 7: K-Map for D<sub>B</sub>

The simplified equation for  $D_B$  is:

$$D_B = (\overline{x_{in}} \cdot B) + (x_{in} \cdot \overline{B} \cdot \overline{A}) + (x_{in} \cdot A \cdot B) \quad (13)$$

Also it can be simplified with XNOR gates as follows:

$$D_B = (\overline{x_{in}} \cdot B) + (x_{in} \cdot (A \odot B)) \quad (14)$$

So the circuit can be implemented as follows:

$$D_A = x_{in} \oplus A \quad (15)$$

$$D_B = (\overline{x_{in}} \cdot B) + (x_{in} \cdot (A \odot B)) \quad (16)$$

#### Question 4

For a serial 2s complemter, the circuit can be implemented as follows:

$S_0$  : We have not seen a 1 yet copy the input to the output

$S_1$  : We have seen a 1, invert the output.

This is for LSB sent first approach.

The finite state machine can be implemented as follows:

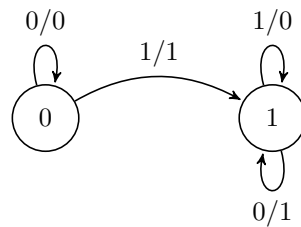


Figure 8: State Diagram

The state table can be written as follows:

Table 7: State Table

Present State		Next State	
Q	x	Q(t+1)	y
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	0

We are using D latch for this implementation. The D input can be written as follows:

It can be seen from the table that the D input is:

$$D = Q + x \quad (17)$$

And it can be seen that the y is the xor of the Q and x:

$$y = Q \oplus x \quad (18)$$

The circuit can be implemented as follows:

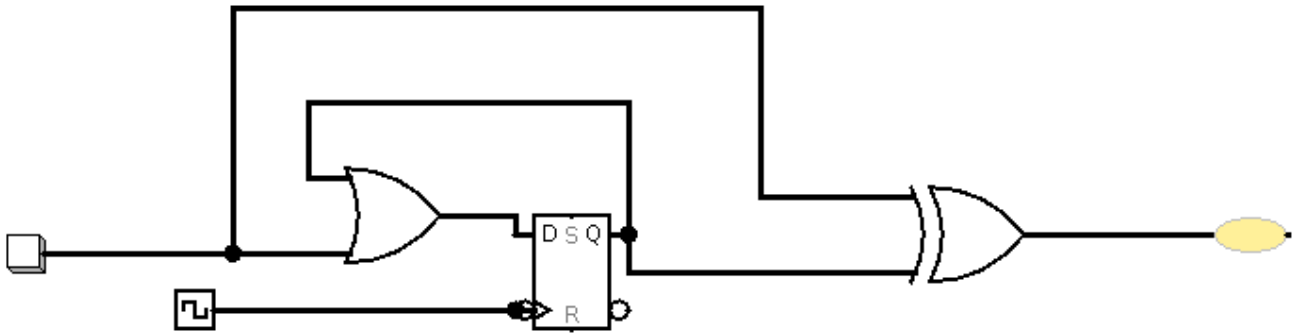


Figure 9: Logic Diagram for the State Machine



## Question 5

The requested state transition table is given in Table 8.

Table 8: State Transition Table for Sequential Circuit

Current State		Inputs		Next State	
A	B	E	F	A*	B*
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	0	1
0	1	1	0	0	0
0	1	1	1	1	0
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	0	1
1	0	1	1	1	1
1	1	0	0	1	1
1	1	0	1	1	1
1	1	1	0	1	0
1	1	1	1	0	0

The state machine diagram can be drawn as follows:

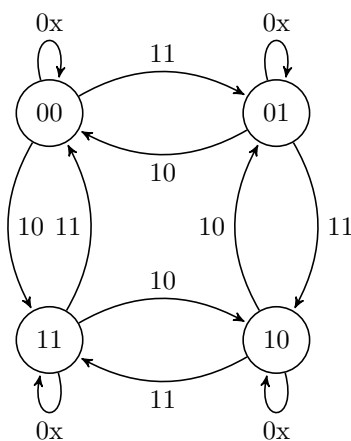


Figure 10: State Diagram

The E signal allows signal to change if its 0 F signal does not matter and the state does not change.

F = 1 counts up the state and F = 0 counts down the state.

The JK flip-flop equations can be written as follows:

$$Q(t+1) = J \cdot \bar{Q} + \bar{K} \cdot Q \quad (19)$$

And the excitation table for the JK flip-flop can be written as follows:

Table 9: JK Flip-Flop Excitation Table

Present State	Next State	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

We can add 4 columns for  $J_A, J_B, K_A, K_B$

Table 10: State Transition Table for Sequential Circuit

Current State		Inputs		Next State		FF Inputs			
A	B	E	F	A*	B*	J_A	K_A	J_B	K_B
0	0	0	0	0	0	0	X	0	X
0	0	0	1	0	0	0	X	0	X
0	0	1	0	1	1	1	X	1	X
0	0	1	1	0	1	0	X	1	X
0	1	0	0	0	1	0	X	X	0
0	1	0	1	0	1	0	X	X	0
0	1	1	0	0	0	0	X	X	1
0	1	1	1	1	0	1	X	X	1
1	0	0	0	1	0	X	0	0	X
1	0	0	1	1	0	X	0	0	X
1	0	1	0	0	1	X	1	1	X
1	0	1	1	1	1	X	0	1	X
1	1	0	0	1	1	X	0	X	0
1	1	0	1	1	1	X	0	X	0
1	1	1	0	1	0	X	0	X	1
1	1	1	1	0	0	X	1	X	1

For finding the equations we can use kmaps:

		$EF$			
		00	01	11	10
$AB$	00	0	0	0	1
	01	0	0	1	0
	11	X	X	X	X
	10	X	X	X	X

Figure 11: K-map for  $J_A$

		$EF$			
		00	01	11	10
$AB$	00	X	X	X	X
	01	X	X	X	X
	11	0	0	1	0
	10	0	0	0	1

Figure 12: K-map for  $K_A$

		$EF$			
		00	01	11	10
$AB$	00	0	0	1	1
	01	X	X	X	X
	11	X	X	X	X
	10	0	0	1	1

Figure 13: K-map for J\_B

		$EF$			
		00	01	11	10
$AB$	00	X	X	X	X
	01	0	0	1	1
	11	0	0	1	1
	10	X	X	X	X

Figure 14: K-map for K\_B

The final equations for the flip flops can be obtained from kmaps as follows:

$$J_A = A'B \cdot (BF + B'F') \quad (20)$$

$$K_A = AE \cdot (BF + B'F') \quad (21)$$

$$J_B = E \quad (22)$$

$$K_B = E \quad (23)$$