

Introduction to Logic Design

EEF205E

Homework 5

Rüzgar Erik
040240783

Istanbul Technical University
Faculty of Electrical and Electronics Engineering

January 11, 2025

Question 1

Recalling the JK flip-flop equations we can derive $A(t+1)$ and $B(t+1)$ as follows:

$$Q(t+1) = J \cdot \overline{Q} + \overline{K} \cdot Q \quad (1)$$

For the A flip-flop: $J_A = x$ and $K_A = b$

$$A(t+1) = x \cdot \overline{A} + \overline{b} \cdot A \quad (2)$$

For the B flip-flop: $J_B = x$ and $K_B = \overline{a}$

$$B(t+1) = x \cdot \overline{B} + a \cdot B \quad (3)$$

Given that there are 2 flip-flops there are $2^2 = 4$ states and we can write the state transition table as follows:

Table 1: State Transition Table

Present State			Next State	
A	B	x	A(t+1)	B(t+1)
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	1	0
1	0	0	1	0
1	0	1	1	1
1	1	0	0	1
1	1	1	0	1

We can draw the state diagram as follows:

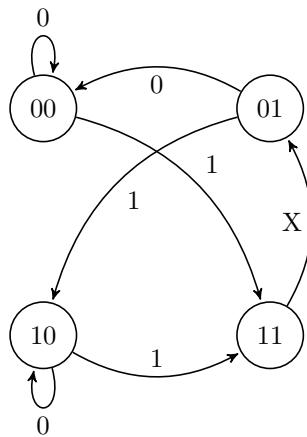


Figure 1: State Diagram

Question 2

The logic diagram for the state machine can be drawn as follows:

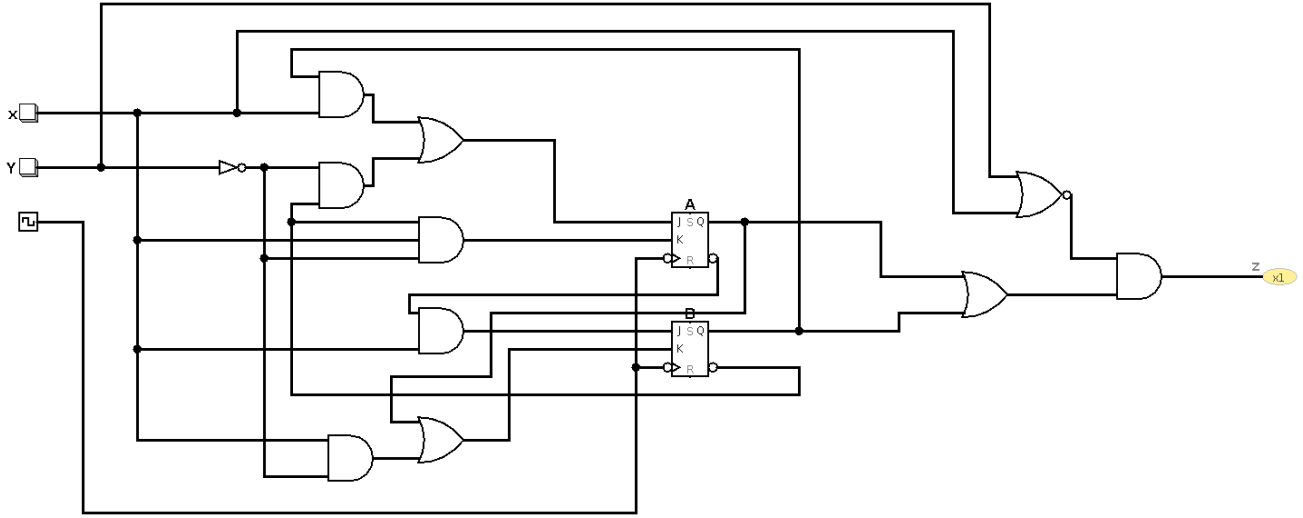


Figure 2: Logic Diagram for the State Machine

The state table can be written as follows:

Figure 3: State Table

Present State				Next State		
A	B	x	y	A*	B*	z
0	0	0	0	1	0	0
0	0	0	1	0	0	0
0	0	1	0	1	1	0
0	0	1	1	0	1	0
0	1	0	0	0	1	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	1	0
1	0	0	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	0
1	0	1	1	1	0	0
1	1	0	0	1	0	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	1	0	0

Recalling the JK flip-flop equations we can derive $A(t+1)$ and $B(t+1)$ as follows:

$$Q(t+1) = J \cdot \overline{Q} + \overline{K} \cdot Q \quad (4)$$

For the A flip-flop:

$$A^* = (b \cdot x + b' \cdot y') \cdot A' + (b + x' + y) \cdot A \quad (5)$$

$$B^* = (a' \cdot x) \cdot B' + [a' \cdot (x' + y)] \cdot B \quad (6)$$

Question 3

Part A

The state table for the requested circuit can be written as follows:

Table 2: State Table

Present State			Next State	
A	B	x	A(t+1)	B(t+1)
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	1
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

To design the circuit with D Flip Flops We need its excitation table:

Table 3: D Flip-Flop Excitation Table

Present State	Next State	D Input
0	0	0
0	1	1
1	0	0
1	1	1

It can be seen that the equation for the D flip-flop is $D = Q(t+1)$ so we can take the next state values from the state table and write the D values as follows:

Table 4: State Table

Present State			Next State		D Inputs	
A	B	x	A(t+1)	B(t+1)	D_A	D_B
0	0	0	0	0	0	0
0	0	1	0	1	0	1
0	1	0	0	1	0	1
0	1	1	1	1	1	1
1	0	0	1	0	1	0
1	0	1	0	0	0	0
1	1	0	1	1	1	1
1	1	1	1	0	1	0

We can find equations for D_A and D_B with the help of kmaps:

		x	
		0	1
AB	00	0	0
	01	0	1
	11	1	1
	10	1	0

Figure 4: K-Map for D_A

The simplified equation for D_A is:

$$D_A = (\overline{x_{in}} \cdot A) + (x_{in} \cdot B) \quad (7)$$

We can draw the K-Map for D_B as follows:

		x	
		0	1
AB	00	0	1
	01	1	1
	11	1	0
	10	0	0

Figure 5: K-Map for D_B

The simplified equation for D_B is:

$$D_B = (\overline{x_{in}} \cdot B) + (x_{in} \cdot \overline{A}) \quad (8)$$

All of the equations can be implemented in a circuit as follows:

$$D_A = (\overline{x_{in}} \cdot A) + (x_{in} \cdot B) \quad (9)$$

$$D_B = (\overline{x_{in}} \cdot B) + (x_{in} \cdot \overline{A}) \quad (10)$$

Part B

The state table for the requested circuit can be written as follows:

Table 5: State Table

Present State			Next State	
A	B	x	A(t+1)	B(t+1)
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	0	0
1	1	0	1	1
1	1	1	0	1

Again using the principle of D flip-flops we can add the D inputs to the state table as follows:

Table 6: State Table

Present State			Next State		D Inputs	
A	B	x	A(t+1)	B(t+1)	D_A	D_B
0	0	0	0	0	0	0
0	0	1	1	1	1	1
0	1	0	0	1	0	1
0	1	1	1	0	1	0
1	0	0	1	0	1	0
1	0	1	0	0	0	0
1	1	0	1	1	1	1
1	1	1	0	1	0	1

We can find equations for D_A and D_B with the help of kmaps:

		x	
		0	1
AB	00	0	1
	01	0	1
	11	1	0
	10	1	0

Figure 6: K-Map for D_A

The simplified equation for D_A is:

$$D_A = (\overline{x_{in}} \cdot A) + (x_{in} \cdot \overline{A}) \quad (11)$$

This shows an XOR gate is needed for the implementation of D_A .

$$D_A = x_{in} \oplus A \quad (12)$$

We can draw the K-Map for D_B as follows:

		x	
		0	1
AB	00	0	1
	01	1	0
	11	1	1
	10	0	0

Figure 7: K-Map for D_B

The simplified equation for D_B is:

$$D_B = (\overline{x_{in}} \cdot B) + (x_{in} \cdot \overline{B} \cdot \overline{A}) + (x_{in} \cdot A \cdot B) \quad (13)$$

Also it can be simplified with XNOR gates as follows:

$$D_B = (\overline{x_{in}} \cdot B) + (x_{in} \cdot (A \odot B)) \quad (14)$$

So the circuit can be implemented as follows:

$$D_A = x_{in} \oplus A \quad (15)$$

$$D_B = (\overline{x_{in}} \cdot B) + (x_{in} \cdot (A \odot B)) \quad (16)$$

Question 4

For a serial 2s complemter, the circuit can be implemented as follows:

S_0 : We have not seen a 1 yet copy the input to the output

S_1 : We have seen a 1, invert the output.

This is for LSB sent first approach.

The finite state machine can be implemented as follows:

 


Figure 8: State Diagram

The state table can be written as follows:

Table 7: State Table

Present State		Next State	
Q	x	Q(t+1)	y
0	0	0	0
0	1	1	1
1	0	1	1
1	1	1	0

We are using D latch for this implementation. The D input can be written as follows:

It can be seen from the table that the D input is:

$$D = Q + x \quad (17)$$

And it can be seen that the y is the xor of the Q and x:

$$y = Q \oplus x \quad (18)$$

The circuit can be implemented as follows:

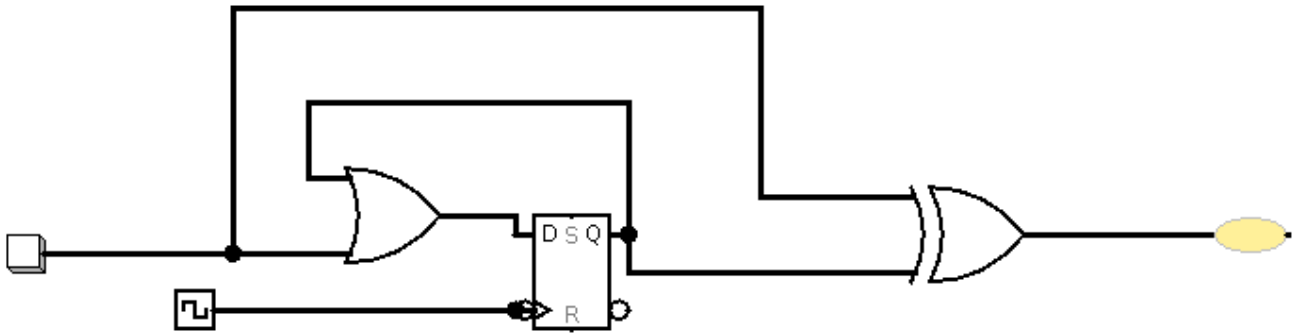


Figure 9: Logic Diagram for the State Machine

Question 5

The requested state transition table is given in Table 8.

Table 8: State Transition Table for Sequential Circuit

Current State		Inputs		Next State	
A	B	E	F	A*	B*
0	0	0	0	0	0
0	0	0	1	0	0
0	0	1	0	1	1
0	0	1	1	0	1
0	1	0	0	0	1
0	1	0	1	0	1
0	1	1	0	0	0
0	1	1	1	1	0
1	0	0	0	1	0
1	0	0	1	1	0
1	0	1	0	0	1
1	0	1	1	1	1
1	1	0	0	1	1
1	1	0	1	1	1
1	1	1	0	1	0
1	1	1	1	0	0

The state machine diagram can be drawn as follows:

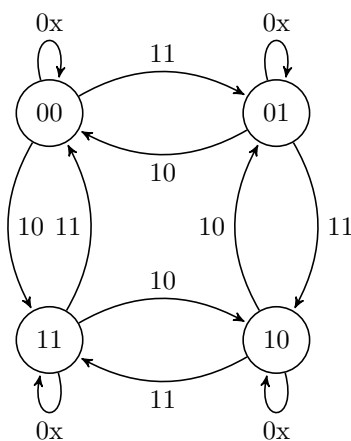


Figure 10: State Diagram

The E signal allows signal to change if its 0 F signal does not matter and the state does not change.

F = 1 counts up the state and F = 0 counts down the state.

The JK flip-flop equations can be written as follows:

$$Q(t+1) = J \cdot \bar{Q} + \bar{K} \cdot Q \quad (19)$$

And the excitation table for the JK flip-flop can be written as follows:

Table 9: JK Flip-Flop Excitation Table

Present State	Next State	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

We can add 4 columns for J_A, J_B, K_A, K_B

Table 10: State Transition Table for Sequential Circuit

Current State		Inputs		Next State		FF Inputs			
A	B	E	F	A*	B*	J_A	K_A	J_B	K_B
0	0	0	0	0	0	0	X	0	X
0	0	0	1	0	0	0	X	0	X
0	0	1	0	1	1	1	X	1	X
0	0	1	1	0	1	0	X	1	X
0	1	0	0	0	1	0	X	X	0
0	1	0	1	0	1	0	X	X	0
0	1	1	0	0	0	0	X	X	1
0	1	1	1	1	0	1	X	X	1
1	0	0	0	1	0	X	0	0	X
1	0	0	1	1	0	X	0	0	X
1	0	1	0	0	1	X	1	1	X
1	0	1	1	1	1	X	0	1	X
1	1	0	0	1	1	X	0	X	0
1	1	0	1	1	1	X	0	X	0
1	1	1	0	1	0	X	0	X	1
1	1	1	1	0	0	X	1	X	1

For finding the equations we can use kmaps:

		EF			
		00	01	11	10
AB	00	0	0	0	1
	01	0	0	1	0
	11	X	X	X	X
	10	X	X	X	X

Figure 11: K-map for J_A

		EF			
		00	01	11	10
AB	00	X	X	X	X
	01	X	X	X	X
	11	0	0	1	0
	10	0	0	0	1

Figure 12: K-map for K_A

		<i>EF</i>			
		00	01	11	10
<i>AB</i>	00	0	0	1	1
	01	X	X	X	X
	11	X	X	X	X
	10	0	0	1	1

Figure 13: K-map for J_B

		<i>EF</i>			
		00	01	11	10
<i>AB</i>	00	X	X	X	X
	01	0	0	1	1
	11	0	0	1	1
	10	X	X	X	X

Figure 14: K-map for K_B

The final equations for the flip flops can be obtained from kmaps as follows:

$$J_A = A'B \cdot (BF + B'F') \quad (20)$$

$$K_A = AE \cdot (BF + B'F') \quad (21)$$

$$J_B = E \quad (22)$$

$$K_B = E \quad (23)$$

Part 2

Question 1

The Vhdl code for the requested circuit can be written as follows:

Listing 1: JK_LATCH.vhd

```

1 library IEEE;
2
3 use IEEE.STD_LOGIC_1164.ALL;
4

```

```

5 entity JK_Latch is
6     Port ( J : in  STD_LOGIC;
7           K : in  STD_LOGIC;
8           EN: in  STD_LOGIC;
9           Q : out  STD_LOGIC;
10          QN : out  STD_LOGIC);
11
12 end JK_Latch;
13
14
15 architecture Behavioral of JK_Latch is
16
17     signal state : STD_LOGIC := '0';
18
19 begin
20     process (J, K, EN)
21     begin
22         if (EN = '1') then
23             if (J = '0' and K = '0') then
24                 state <= state;
25             elsif (J = '0' and K = '1') then
26                 state <= '0';
27             elsif (J = '1' and K = '0') then
28                 state <= '1';
29             elsif (J = '1' and K = '1') then
30                 state <= not state;
31             end if;
32         end if;
33     end process;
34
35     Q <= state;
36     QN <= not state;
37
38 end Behavioral;

```

The testbench for the requested circuit can be written as follows:

Listing 2: JK_LATCH_tb.vhd

```

1 library IEEE;
2
3 use IEEE.STD_LOGIC_1164.ALL;
4
5 entity JK_Latch_tb is
6 end JK_Latch_tb;
7
8 architecture Behavioral of JK_Latch_tb is
9
10     component JK_Latch
11         Port ( J : in  STD_LOGIC;
12               K : in  STD_LOGIC;
13               EN: in  STD_LOGIC;
14               Q : out  STD_LOGIC;
15               QN : out  STD_LOGIC);
16     end component;
17
18     signal JTB : STD_LOGIC := '0';
19     signal KTB : STD_LOGIC := '0';
20     signal ENTB : STD_LOGIC := '0';
21     signal QTB : STD_LOGIC;
22     signal QNTB : STD_LOGIC;
23

```

```
24 begin
25
26     UUT: JK_Latch port map (J => JTB, K => KTB, EN => ENTB, Q => QTB, Q
27
28     stim_proc: process
29     begin
30
31         -- Initial state
32
33         JTB <= '0';
34         KTB <= '0';
35         ENTB <= '0';
36         wait for 100 ns;
37
38
39         -- No change expected
40         ENTB <= '1';
41         JTB <= '0';
42         KTB <= '0';
43         wait for 100 ns;
44
45         -- Q = 1
46         ENTB <= '1';
47         JTB <= '1';
48         KTB <= '0';
49         wait for 100 ns;
50
51         -- Q = 0
52         ENTB <= '1';
53         JTB <= '0';
54         KTB <= '1';
55         wait for 100 ns;
56
57
58         -- Toggle
59
60         ENTB <= '1';
61         JTB <= '1';
62         KTB <= '1';
63         wait for 100 ns;
64
65         wait;
66     end process;
67
68 end Behavioral;
```

The RTL schematic for the requested circuit can be seen in Figure 15.

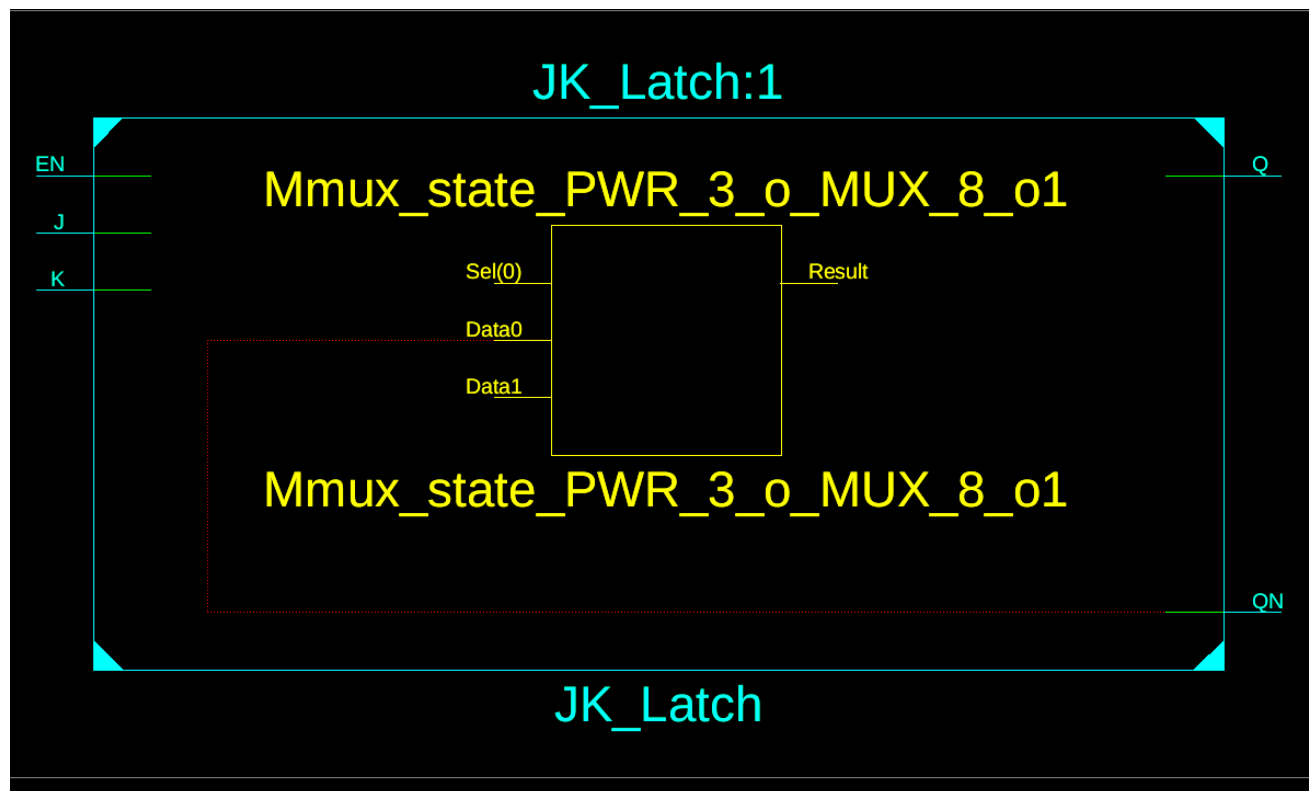


Figure 15: RTL Schematic for JK Latch

The simulation results can be seen in Figure 16.

 


Figure 16: Simulation Results for JK Latch

Question 2

The Vhdl code for the requested circuit can be written as follows:

Listing 3: JK_FF.vhd

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity JK_FF is
5      Port (
6          J : in STD_LOGIC;
7          K : in STD_LOGIC;
8          CLK : in STD_LOGIC;
9          Q : out STD_LOGIC;
10         QN : out STD_LOGIC
11     );
12 end JK_FF;
13
14 architecture Behavioral of JK_FF is
15     signal state : STD_LOGIC := '0';
16 begin
17

```

```

18     process(CLK)
19     begin
20         if rising_edge(CLK) then
21             if J = '0' and K = '0' then
22                 state <= state;
23             elsif J = '0' and K = '1' then
24                 state <= '0';
25             elsif J = '1' and K = '0' then
26                 state <= '1';
27             elsif J = '1' and K = '1' then
28                 state <= not state;
29             end if;
30         end if;
31     end process;
32
33     Q <= state;
34     QN <= not state;
35
36 end Behavioral;

```

The testbench for the requested circuit can be written as follows:

Listing 4: JK_FF_tb.vhd

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity JK_FF_TB is
5  end JK_FF_TB;
6
7  architecture Behavioral of JK_FF_TB is
8
9      component JK_FF
10         Port ( J : in  STD_LOGIC;
11               K : in  STD_LOGIC;
12               CLK: in  STD_LOGIC;
13               Q  : out STD_LOGIC;
14               QN : out STD_LOGIC);
15     end component;
16
17     signal JTB : STD_LOGIC := '0';
18     signal KTB : STD_LOGIC := '0';
19     signal CLKTB : STD_LOGIC := '0';
20     signal QTB : STD_LOGIC;
21     signal QNTB : STD_LOGIC;
22
23 begin
24
25     UUT: JK_FF port map (J => JTB, K => KTB, CLK => CLKTB, Q => QTB, QN => QNTB);
26
27     clock : process
28     begin
29         CLKTB <= '0';
30         wait for 5 ns;
31         CLKTB <= '1';
32         wait for 5 ns;
33     end process;
34
35     stim_proc: process
36     begin
37         JTB <= '0';
38         KTB <= '0';

```

```

39         wait for 100 ns;
40
41         JTB <= '0';
42         KTB <= '0';
43         wait for 100 ns;
44
45         JTB <= '1';
46         KTB <= '0';
47         wait for 100 ns;
48
49         JTB <= '0';
50         KTB <= '1';
51         wait for 100 ns;
52
53         JTB <= '1';
54         KTB <= '1';
55         wait for 100 ns;
56
57         wait;
58     end process;
59
60 end Behavioral;

```

The RTL schematic for the requested circuit can be seen in Figure 17.

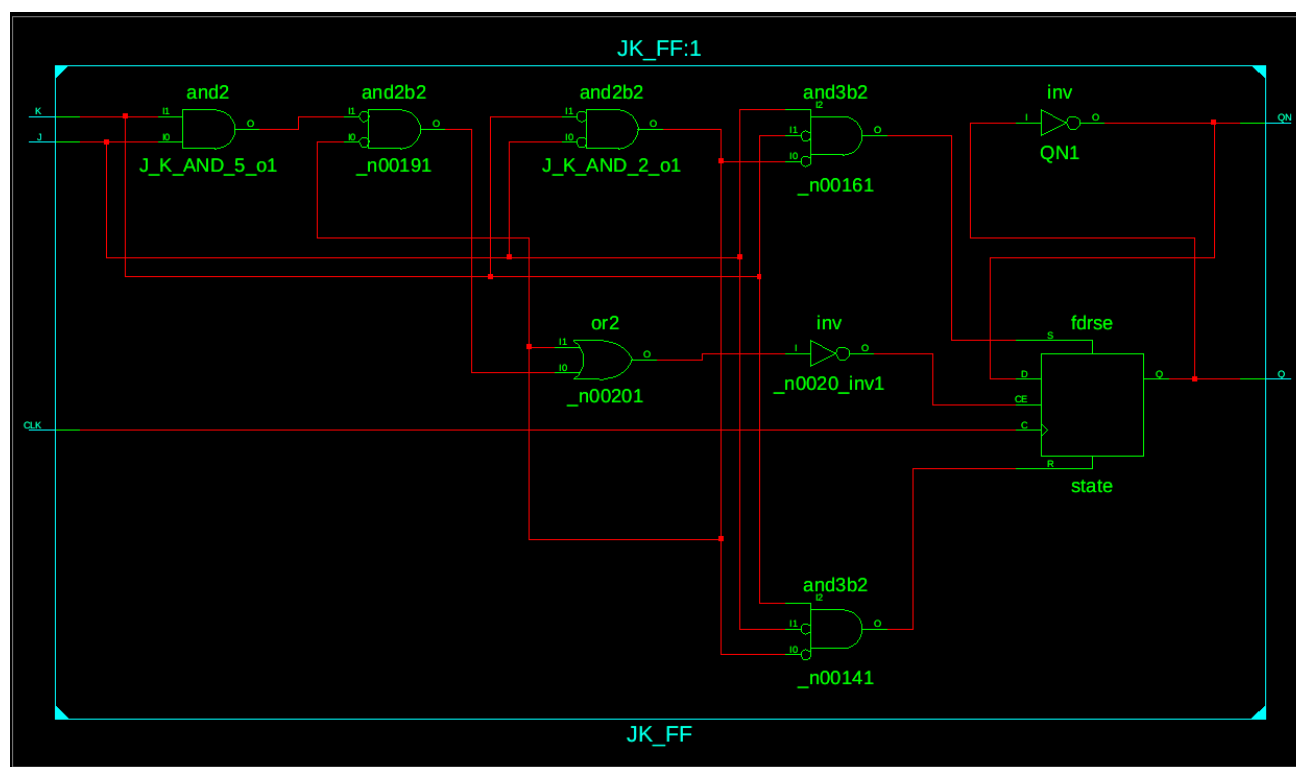


Figure 17: RTL Schematic for JK Flip Flop

The simulation results can be seen in Figure 18.

 


Figure 18: Simulation Results for JK Flip Flop

Question 3

 


Figure 19: State Diagram for Pattern Detector

1. **S0**: Initial state (waiting for a valid start of a pattern).
2. **S1**: '10' detected (beginning of Pattern 1).
3. **S2**: '10-10' detected (middle of Pattern 1).
4. **S3**: '10-10-11' detected (Pattern 1 complete, $Z = 1$).
5. **S4**: '11' detected (beginning of Pattern 2).
6. **S5**: '11-00' detected (middle of Pattern 2).
7. **S6**: '11-00-01' detected (Pattern 2 complete, $Z = 1$).

The VHDL code for the requested circuit can be written as follows:

Listing 5: Pattern_Detector.vhd

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity Pattern_Detector is
5      Port (
6          CLK : in STD_LOGIC;
7          DATA_IN : in STD_LOGIC_VECTOR(1 downto 0);
8          Z : out STD_LOGIC
9      );
10 end Pattern_Detector;
11
12 architecture Behavioral of Pattern_Detector is
13     type state_type is (S0, S1, S2, S3, S4, S5, S6);
14     signal STATE_CURRENT, STATE_NEXT : state_type := S0;
15     signal Z_internal : STD_LOGIC := '0';
16 begin
17     process (CLK)
18     begin
19         if rising_edge(CLK) then
20             STATE_CURRENT <= STATE_NEXT;

```

```

21         Z <= Z_internal;
22     end if;
23 end process;
24
25 process (STATE_CURRENT, DATA_IN)
26 begin
27     STATE_NEXT <= S0;
28     Z_internal <= '0';
29
30     case STATE_CURRENT is
31     when S0 =>
32         if DATA_IN = "10" then
33             STATE_NEXT <= S1;
34         elsif DATA_IN = "11" then
35             STATE_NEXT <= S4;
36         end if;
37
38     when S1 =>
39         if DATA_IN = "10" then
40             STATE_NEXT <= S2;
41         else
42             STATE_NEXT <= S0;
43         end if;
44
45     when S2 =>
46         if DATA_IN = "11" then
47             STATE_NEXT <= S3;
48             Z_internal <= '1';
49         else
50             STATE_NEXT <= S0;
51         end if;
52
53     when S3 =>
54         STATE_NEXT <= S0;
55
56     when S4 =>
57         if DATA_IN = "00" then
58             STATE_NEXT <= S5;
59         else
60             STATE_NEXT <= S0;
61         end if;
62
63     when S5 =>
64         if DATA_IN = "01" then
65             STATE_NEXT <= S6;
66             Z_internal <= '1';
67         else
68             STATE_NEXT <= S0;
69         end if;
70
71     when S6 =>
72         STATE_NEXT <= S0;
73
74     when others =>
75         STATE_NEXT <= S0;
76     end case;
77 end process;
78 end Behavioral;

```

The testbench for the requested circuit can be written as follows:

Listing 6: Pattern_Detector_tb.vhd

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity Pattern_Detector_tb is
5  end Pattern_Detector_tb;
6
7  architecture Behavioral of Pattern_Detector_tb is
8      signal CLK : STD_LOGIC := '0';
9      signal DATA_IN : STD_LOGIC_VECTOR(1 downto 0) := "00";
10     signal Z : STD_LOGIC;
11
12     component Pattern_Detector is
13         Port (
14             CLK : in STD_LOGIC;
15             DATA_IN : in STD_LOGIC_VECTOR(1 downto 0);
16             Z : out STD_LOGIC
17         );
18     end component;
19
20 begin
21     uut: Pattern_Detector
22         port map (
23             CLK => CLK,
24             DATA_IN => DATA_IN,
25             Z => Z
26         );
27
28     clock : process
29     begin
30         while true loop
31             CLK <= '0';
32             wait for 5 ns;
33             CLK <= '1';
34             wait for 5 ns;
35         end loop;
36     end process;
37
38     process
39     begin
40         wait for 10 ns;
41         DATA_IN <= "00";
42         wait for 10 ns;
43         DATA_IN <= "10";
44         wait for 10 ns;
45         DATA_IN <= "10";
46         wait for 10 ns;
47         DATA_IN <= "11";
48         wait for 10 ns;
49         DATA_IN <= "01";
50         wait for 10 ns;
51         DATA_IN <= "10";
52         wait for 10 ns;
53         DATA_IN <= "11";
54         wait for 10 ns;
55         DATA_IN <= "00";
56         wait for 10 ns;
57         DATA_IN <= "01";
58         wait for 10 ns;
59         DATA_IN <= "00";
60         wait for 10 ns;

```

```
61     DATA_IN <= "10";
62     wait for 10 ns;
63     DATA_IN <= "00";
64     wait for 10 ns;
65     DATA_IN <= "10";
66     wait for 10 ns;
67     DATA_IN <= "10";
68     wait for 10 ns;
69     DATA_IN <= "11";
70     wait for 10 ns;
71     DATA_IN <= "10";
72     wait for 10 ns;
73     DATA_IN <= "10";
74     wait for 10 ns;
75     DATA_IN <= "11";
76     wait for 10 ns;
77     wait;
78     end process;
79
80 end Behavioral;
```

The RTL schematic for the requested circuit can be seen in Figure 20.

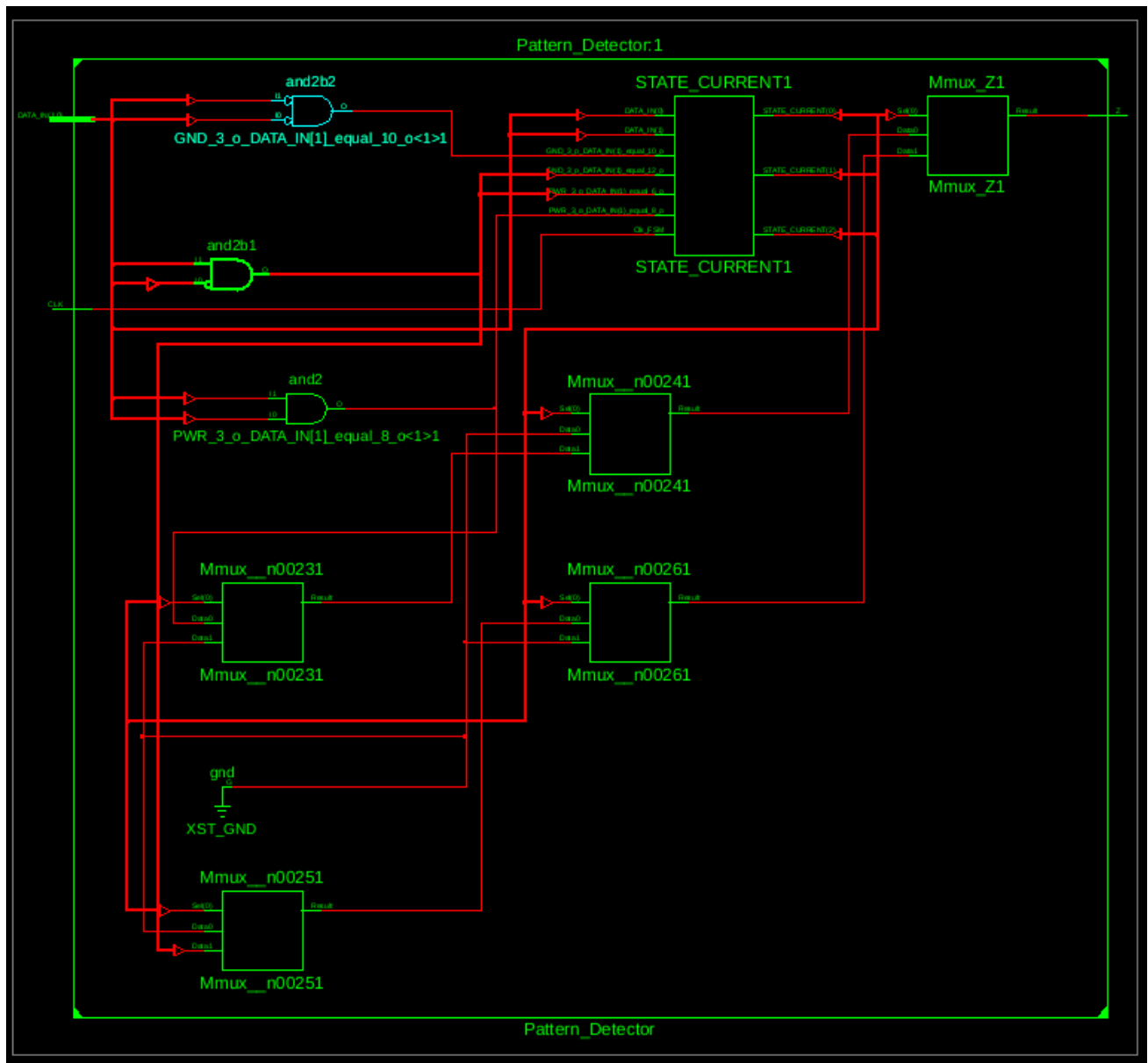


Figure 20: RTL Schematic for Pattern Detector

The simulation results can be seen in Figure 21.

 


Figure 21: Simulation Results for Pattern Detector

Question 4

Assigning the states as follows:

Table 11: State and Assignment Table

State	$Q_2Q_1Q_0$
S_0	000
S_1	001
S_2	010
S_3	011
S_4	100
S_5	101
S_6	110

Using the excitation table of JK flip-flops, we can find the JK inputs for each state transition as follows:

Table 12: JK Flip-Flop Excitation Table

Present State	Next State	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Current ($Q_2Q_1Q_0$)	Input (A_1A_0)	Next ($Q_2^+Q_1^+Q_0^+$)	Z	(J_2, K_2)	(J_1, K_1)	(J_0, K_0)
000 (S_0)	10	001 (S_1)	0	(0, X)	(0, X)	(1, X)
000 (S_0)	11	100 (S_4)	0	(1, X)	(0, X)	(0, X)
000 (S_0)	Others	000 (S_0)	0	(0, X)	(0, X)	(0, X)
001 (S_1)	10	010 (S_2)	0	(0, X)	(1, X)	(X, 1)
001 (S_1)	Others	000 (S_0)	0	(0, X)	(0, X)	(X, 1)
010 (S_2)	11	011 (S_3)	1	(0, X)	(X, 0)	(1, X)
010 (S_2)	Others	000 (S_0)	0	(0, X)	(X, 1)	(0, X)
011 (S_3)	Any	000 (S_0)	0	(0, X)	(X, 1)	(X, 1)
100 (S_4)	00	101 (S_5)	0	(X, 0)	(0, X)	(1, X)
100 (S_4)	Others	000 (S_0)	0	(X, 1)	(0, X)	(0, X)
101 (S_5)	01	110 (S_6)	1	(X, 0)	(1, X)	(X, 1)
101 (S_5)	Others	000 (S_0)	0	(X, 1)	(0, X)	(X, 1)
110 (S_6)	Any	000 (S_0)	0	(X, 1)	(X, 1)	(0, X)

Table 13: State Transition Table with JK Inputs

The expressions were simplified and the results are

$$\begin{aligned}
J_2 &= \overline{Q_2} \overline{Q_1} \overline{Q_0} A_1 A_0, \\
K_2 &= (Q_2 Q_1) + (Q_2 \overline{Q_1} \overline{Q_0} (A_1 + A_0)) + (Q_2 \overline{Q_1} Q_0 (A_1 + \overline{A_0})), \\
J_1 &= \overline{Q_1} Q_0 (\overline{Q_2} A_1 \overline{A_0} + Q_2 \overline{A_1} A_0), \\
K_1 &= \overline{Q_2} Q_1 \overline{Q_0} (\overline{A_1} + \overline{A_0}) + \overline{Q_2} Q_1 Q_0 + Q_2 Q_1 \overline{Q_0}, \\
J_0 &= \overline{Q_2} \overline{Q_1} \overline{Q_0} A_1 \overline{A_0} + \overline{Q_2} Q_1 \overline{Q_0} A_1 A_0 + Q_2 \overline{Q_1} \overline{Q_0} \overline{A_1} \overline{A_0}, \\
K_0 &= \overline{Q_2} \overline{Q_1} Q_0 (\overline{A_1} + A_0) + \overline{Q_2} Q_1 Q_0 + Q_2 \overline{Q_1} Q_0, \\
Z &= \overline{Q_2} Q_1 \overline{Q_0} A_1 A_0 + Q_2 \overline{Q_1} Q_0 \overline{A_1} A_0.
\end{aligned}$$

The vhdl code for the requested circuit can be written as follows:

Listing 7: Pattern_Detector_JK_FF.vhd

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity sequence_detector is
5      Port (
6          clk      : in  STD_LOGIC;
7          A1       : in  STD_LOGIC;
8          A0       : in  STD_LOGIC;
9          Z        : out STD_LOGIC
10     );
11 end sequence_detector;
12
13 architecture Behavioral of sequence_detector is
14     component JK_FF
15         Port (
16             J      : in  STD_LOGIC;
17             K      : in  STD_LOGIC;
18             CLK    : in  STD_LOGIC;
19             Q      : out STD_LOGIC;
20             QN     : out STD_LOGIC
21         );
22     end component;
23
24     signal Q2, Q1, Q0 : STD_LOGIC;
25     signal QN2, QN1, QN0 : STD_LOGIC;
26     signal J2, K2, J1, K1, J0, K0 : STD_LOGIC;
27
28 begin
29     J2 <= (not Q2) and (not Q1) and (not Q0) and A1 and A0;
30
31     K2 <= (Q2 and Q1) or
32           (Q2 and (not Q1) and (not Q0) and (A1 or A0)) or
33           (Q2 and (not Q1) and Q0 and (A1 or (not A0)));
34
35     J1 <= (not Q1) and Q0 and
36           ((not Q2 and A1 and (not A0)) or (Q2 and (not A1) and A0));
37
38     K1 <= ((not Q2) and Q1 and (not Q0) and ((not A1) or (not A0))) or
39           ((not Q2) and Q1 and Q0) or
40           (Q2 and Q1 and (not Q0));
41
42     J0 <= ((not Q2) and (not Q1) and (not Q0) and A1 and (not A0)) or
43           ((not Q2) and Q1 and (not Q0) and A1 and A0) or
44           (Q2 and (not Q1) and (not Q0) and (not A1) and (not A0));
45
46     K0 <= ((not Q2) and (not Q1) and Q0 and ((not A1) or A0)) or
47           ((not Q2) and Q1 and Q0) or
48           (Q2 and (not Q1) and Q0);
49
50     Z <= ((not Q2) and Q1 and (not Q0) and A1 and A0) or
51           (Q2 and (not Q1) and Q0 and (not A1) and A0);
52
53     FF2: JK_FF port map (
54         J => J2,
55         K => K2,
56         CLK => clk,
57         Q => Q2,
58         QN => QN2
59     );
60

```

```

61     FF1: JK_FF port map (
62         J => J1,
63         K => K1,
64         CLK => clk,
65         Q => Q1,
66         QN => QN1
67     );
68
69     FF0: JK_FF port map (
70         J => J0,
71         K => K0,
72         CLK => clk,
73         Q => Q0,
74         QN => QN0
75     );
76
77 end Behavioral;

```

The testbench for the requested circuit can be written as follows:

Listing 8: Pattern_Detector_JK_FF_tb.vhd

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity sequence_detector_tb is
5  end sequence_detector_tb;
6
7  architecture Behavioral of sequence_detector_tb is
8      signal CLK : STD_LOGIC := '0';
9      signal A1 : STD_LOGIC := '0';
10     signal A0 : STD_LOGIC := '0';
11     signal Z : STD_LOGIC;
12
13     component sequence_detector is
14         Port (
15             clk : in  STD_LOGIC;
16             A1 : in  STD_LOGIC;
17             A0 : in  STD_LOGIC;
18             Z : out STD_LOGIC
19         );
20     end component;
21
22 begin
23     uut: sequence_detector
24         port map (
25             clk => CLK,
26             A1 => A1,
27             A0 => A0,
28             Z  => Z
29         );
30
31     clock : process
32     begin
33         while true loop
34             CLK <= '0';
35             wait for 10 ns;
36             CLK <= '1';
37             wait for 10 ns;
38         end loop;
39     end process;
40

```



```
41 stimulus : process
42 begin
43     wait for 20 ns;
44     A1 <= '1'; A0 <= '0'; wait for 20 ns;
45     A1 <= '1'; A0 <= '0'; wait for 20 ns;
46     A1 <= '1'; A0 <= '1'; wait for 20 ns;
47     A1 <= '1'; A0 <= '1'; wait for 20 ns;
48     A1 <= '0'; A0 <= '0'; wait for 20 ns;
49     A1 <= '0'; A0 <= '1'; wait for 20 ns;
50     A1 <= '0'; A0 <= '0'; wait for 20 ns;
51     A1 <= '1'; A0 <= '0'; wait for 20 ns;
52     A1 <= '1'; A0 <= '0'; wait for 20 ns;
53     A1 <= '1'; A0 <= '1'; wait for 20 ns;
54     A1 <= '1'; A0 <= '0'; wait for 20 ns;
55     A1 <= '1'; A0 <= '0'; wait for 20 ns;
56     A1 <= '1'; A0 <= '1'; wait for 20 ns;
57     wait;
58 end process;
59
60 end Behavioral;
```

The RTL schematic for the requested circuit can be seen in Figure 22.

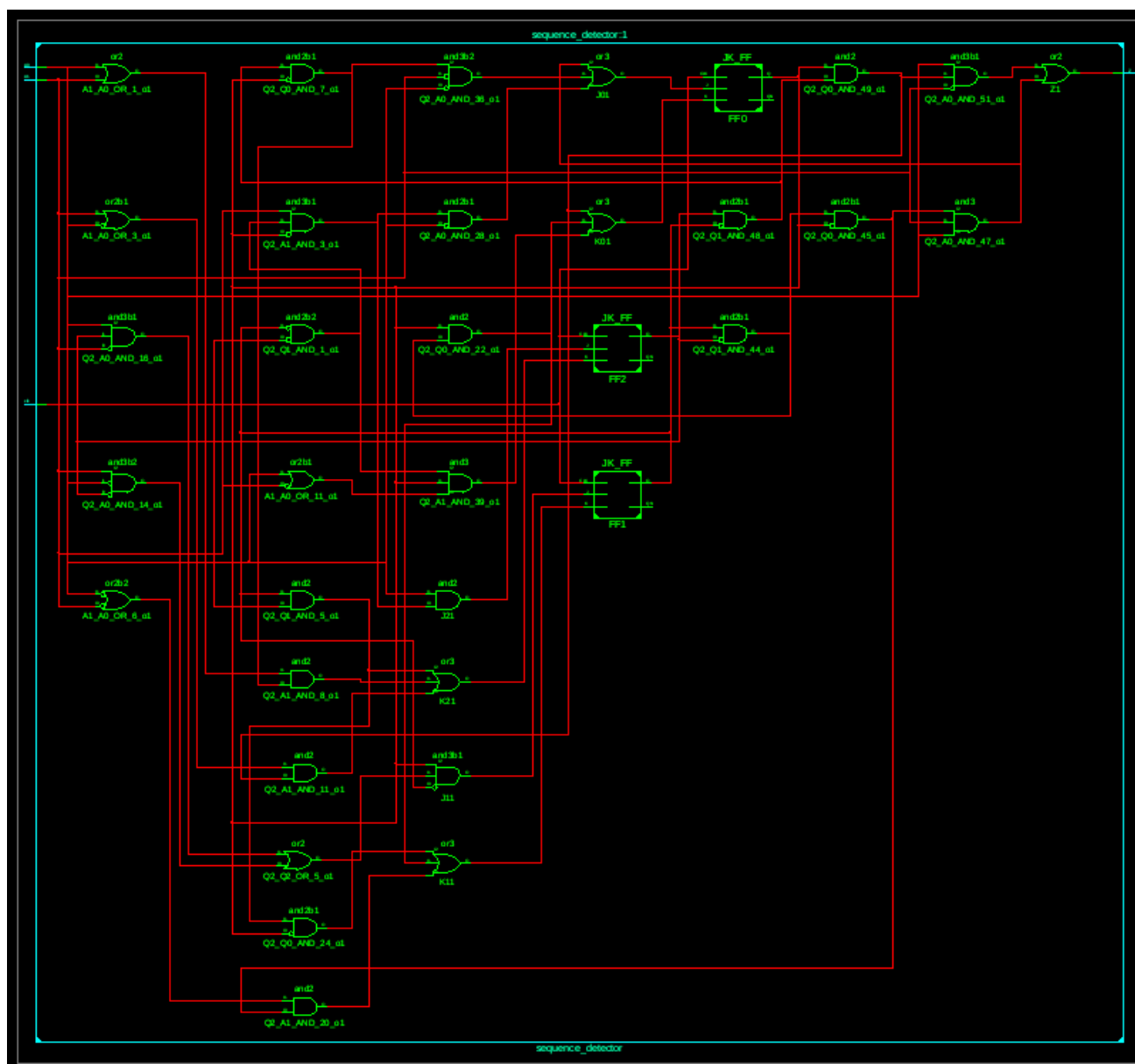


Figure 22: RTL Schematic for Pattern Detector with JK Flip-Flops

The simulation results can be seen in Figure 23.

 


Figure 23: Simulation Results for Pattern Detector with JK Flip-Flops